

DIGITAL SYSTEMS DESIGN

ASSIGNMENT - 1

REPORT SUBMISSION FOR ASSIGNMENT-1

NAME: SWETANG KRISHNA


STUDENT ID: 21355087

CONTENT	PAGE
2'S COMPLIMENT FORM FOR 6-BIT BINARY NUMBER	2
MAIN CIRCUIT DESIGN (FIG-1)	3
SUB CIRCUIT DESIGN FOR MODULE NEGATIVE(FIG-3) & GREATER THAN MODULE	4
CIRCUIT DESIGN FOR RIPPLE ADDER MODULE(FIG-5)	5
CODE FOR TOP LEVEL MODULE (main_ALU_KRISHNA_code)	6
CODE FOR TOP LEVEL MODULE (main_ALU_KRISHNA_code)	7
CODE FOR MODULE NEGATIVE	8
CODE FOR MODULE GR1	9
CODE FOR MODULE GR6	10
CODE FOR MODULE XNOR1 AND XNOR6	11
CODE FOR MODULE FULL_ADDER AND SIX_BIT_ADDER	12-13
VIVADO SCREENSHOTS for different functions	14-18
CODE FOR TESTBENCH	19
TESTBENCH SCREENSHOT	20
TESTBENCH RESULTS and file directory screenshot	21
DEMO	22
PINS ASSIGNED IN FPGA BOARD	23-24
XDC FILE CODE	25-28
OUTPUTS SHOWN ON FPGA BOARD	29
OUTPUTS FOR UNEXPECTED INPUTS	30


DECIMAL	BINARY	DECIMAL	BINARY
-32	100000	0	000000
-31	100001	1	000001
-30	100010	2	000010
-29	100011	3	000011
-28	100100	4	000100
-27	100101	5	000101
-26	100110	6	000110
-25	100111	7	000111
-24	101000	8	001000
-23	101001	9	001001
-22	101010	10	001010
-21	101011	11	001011
-20	101100	12	001100
-19	101101	13	001101
-18	101110	14	001110
-17	101111	15	001111
-16	110000	16	010000
-15	110001	17	010001
-14	110010	18	010010
-13	110011	19	010011
-12	110100	20	010100
-11	110101	21	010101
-10	110110	22	010110
-9	110111	23	010111
-8	111000	24	011000
-7	111001	25	011001
-6	111010	26	011010
-5	111011	27	011011
-4	111100	28	011100
-3	111101	29	011101
-2	111110	30	011110
-1	111111	31	011111

CIRCUIT DESIGN:


MAIN CIRCUIT-> (fig 1)

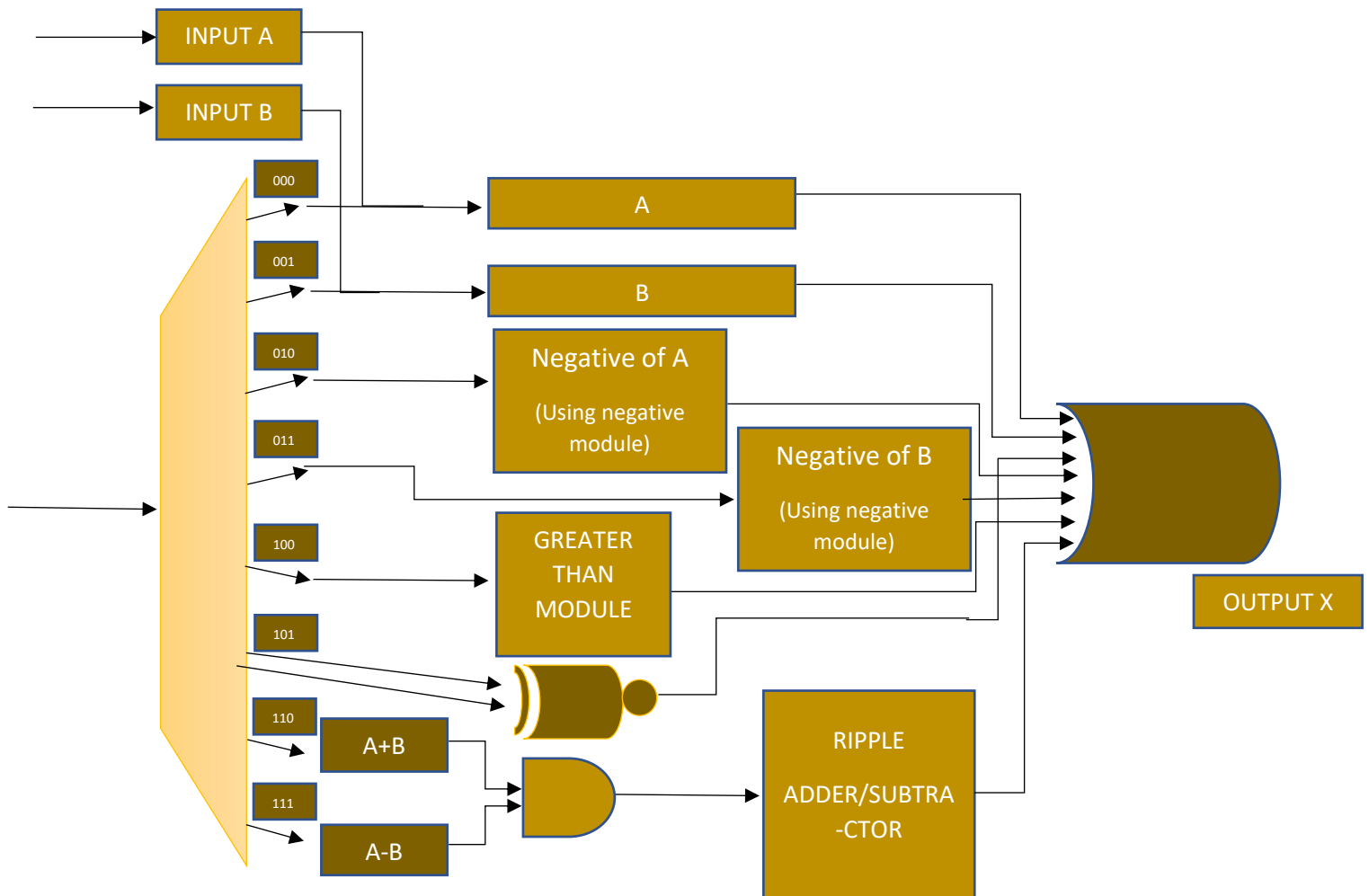


negative of A-> (fig2)

 

negative of B-> (fig 3)

 

Greater than module-> (fig4)

 


FOR A < B the Boolean expression is:

$$B[5]A[5] + X5.(B[4].A[4]) + X5.X4.(B[3].A[3]) + X5.X4.X3(B[2].A[2]) + X5.X4.X3.X2.(B[1].A[1]) + X5.X4.X3.X2.X1.(B[0].A[0])$$

NOTE: Text in red depicts complement of the number

RIPPLE ADDER MODULE->(fig 5)

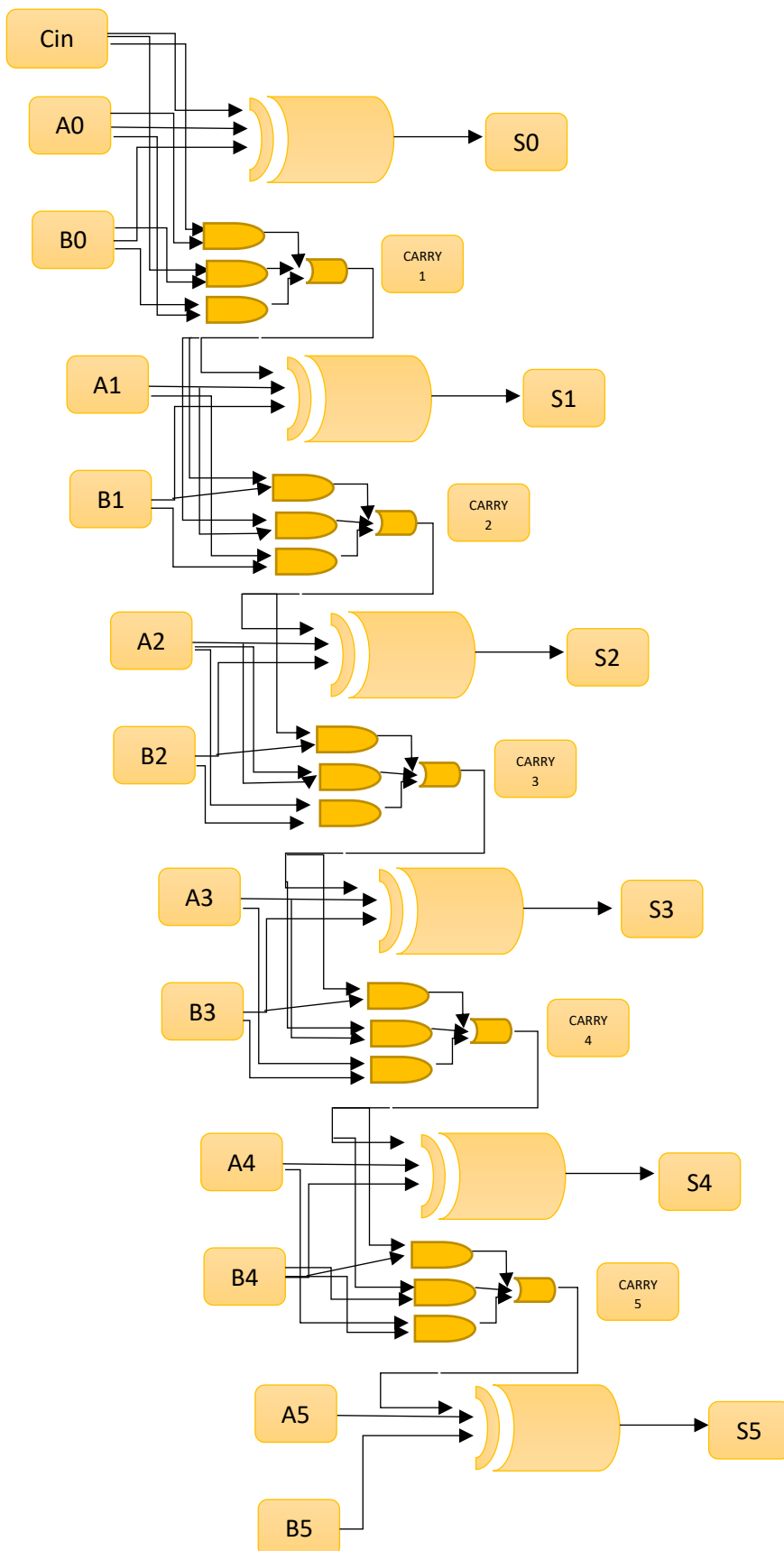

And for subtraction we can use:

$$X = A - B.$$

CODE (top level – ALU module)

```
Module ALU_KRISHNA(
```

```
Input wire[5:0] A,B,
```

```
Output wire[5:0]X
```

```
);
```

```
Wire[5:0] NEG_A,NEG_B,
```

```
XNOR_A_B;
```

```
Wire agrb;
```

```
Wire add_a_b
```

```
Negative neg_A(.m(A),  
.nega(NEG_A));
```

```
Negative neg_B(.m(B),  
.nega(NEG_B));
```

```
Gr6  
greater(.x(A),.y(B),.gr(agrb));
```

```
XNOR6  
constraints_XNOR(.j0(A),.j1(B),  
.k(XNOR_A_B));
```

```
//this module is the main module.
```

```
//inputs 'A' and 'B' are 6-bit numbers.
```

```
//output is a 6-bit number as well.
```

```
// 'NEG_A' & 'NEG_B' stores the negative  
//values of A & B respectively.
```

```
//'XOR_A_B' stores the value of '~(A ^ B)'.
```

```
//agrb stores the value 0 or 1 depending  
//upon whether 'a<b' or 'a>b'.
```

```
//'add_a_b' stores the value of 'A+B'.
```

```
//using module negative we get negative  
//of number 'A' and storing it in 'NEG_A'.
```

```
// using module negative we get negative  
//of number 'B' and storing it in 'NEG_B'.
```

```
//using 'Gr6' module to check whether  
//'A<B'and storing the output in 'agrb'.
```

```
//using 'XNOR' module to find '~(a ^ b)'  
//and storing the value in 'XNOR_A_B'.
```

```
Adder_6_bit
constraints_adder(.x(A),.y(B),
.z(add_a_b));
```

```
//using 'adder_6_bit' module to find 'a+b'
//and storing the output in 'add_a_b'.
```

```
Always@ (*)
```

```
//using demux to find what operation
//must be performed.
```

```
Begin
```

```
    Case(fxn)
```

```
        3'b000:{X}= {A};
```

```
//if fxn = 000 then output is 'A'.
```

```
        3'b001:{X}= {B};
```

```
// if fxn = 001 then output is 'B'.
```

```
        3'b010:{X}= {NEG_A};
```

```
// if fxn = 010 then output is '-A'.
```

```
        3'b011:{X}= {NEG_B};
```

```
// if fxn = 011 then output is '-B'.
```

```
        3'b100:{X}= {agrb};
```

```
// if fxn = 100 then output is 'agrb'.
```

```
        3'b101:{X}= {XNOR_A_B};
```

```
// if fxn = 101 then output is 'XNOR_A_B'.
```

```
        3'b110:{X}= {add_a_b};
```

```
// if fxn = 110 then output is 'add_a_b'.
```

```
        3'b111:{X}= {A-B};
```

```
// if fxn = 111 then output is 'A-B'.
```

```
        Default: {X} = {0};
```

```
// if no input is given the output will be 0.
```

```
    Endcase
```

```
end
```

```
Endmodule
```

Other modules Used->

Module negative

(input wire[5:0] m,

Output wire[5:0] nega

);

Wire[5:0] temp = 6'd0;

always@ (*)

neg = ~((m - 1) ^ temp);

Endmodule

//this module finds the negative of a 6-bit
//number in 2's complement form.

//'m' is the number whose negative is to
//be found.

//the negative of the number will be
//stored in 'nega'.

//'temp' is a 000000 to help us find the 1's
//compliment.

//in order to find the negative, we first
//need to subtract 1 from the LSB then
//find //its XOR with temp and then find
//the negation of the result.

Module gr1

(

input wire i0,i1,

output wire gr

);

Wire p0,p1;

Assign gr = p0 | p1;

Assign p0 = ~i0 & ~i1;

Assign p1 = i0 & i1;

Endmodule

//using gr1 module to find 'Xi' where,

// $X_i = \sim A[0].B[0] + A[0].\sim B[0]$ which we
//will further use to find if $A < B$.

//'i0' and 'i1' are the input single bits.

//'gr' is the final output which is true for
 $A < B$.

//'gr' is true for either 'p0' or 'p1'.

//'p0' and 'p1' will be true if 'i0' and 'i1'
//are equal.

```

Module gr6(
Input wire[5:0] x,y,
Output wire final_bit
);

Wire [5:0] gr_out;
Wire[5:0] out;

Gr1
gr_bit5_unit(.i0(x[5]),.i1(y[5]),.gr(out[5]));

Gr1
gr_bit4_unit(.i0(x[4]),.i1(y[4]),.gr(out[4]));

Gr1
gr_bit3_unit(.i0(x[3]),.i1(y[3]),.gr(out[3]));

Gr1
gr_bit2_unit(.i0(x[2]),.i1(y[2]),.gr(out[2]));

Gr1
gr_bit1_unit(.i0(x[1]),.i1(y[1]),.gr(out[1]));

Assign gr = x[5]&~y[5] |
out[5]&(y[4]&~x[4]) |
out[5]&out[4]&(y[3]&~x[3]) |
out[5]&out[4]&out[3]&(y[2]&~x[2]) |
out[5]&out[4]&out[3]&out[2]&(y[1]&~x[1]) |
out[5]&out[4]&out[3]&out[2]&out[1]&(y[0]&~x[0]);

endmodule

```

//module gr6 is used to find if a 6-bit
//number is greater than the other.

//numbers x and y are to be compared.

//the final out put gr will be a single bit
number.

//out is a 6-bit number which will be 1 if
//the digits compared are equal.

//using gr1 module to find equality for
//each digit.

//further following this process for every
//digit.

//The final output is the sum of products,
//that is described in circuit diagram
//(fig-4).

```

Module XNOR1(
Input wire j0,j1,
Output wire k
);
Assign k = ~(j0 ^ j1);
Endmodule;

```

```

//module XNOR1 will find the answer to
//the expression  $X = \sim(A \wedge B)$ ;

```

```

Module XNOR6(
Input wire[5:0] f,g,
Output wire[5:0] h
);

XNOR1
ans_bit0_unit(.j0(f[0]),.j1(g[0]),..k(h[
0]));

XNOR1
ans_bit1_unit(.j0(f[1]),.j1(g[1]),.k(h[
1]));

XNOR1
ans_bit2_unit(.j0(f[2]),.j1(g[2]),.k(h[
2]));

XNOR1
ans_bit3_unit(.j0(f[3]),.j1(g[3]),.k(h[
3]));

XNOR1
ans_bit4_unit(.j0(f[4]),.j1(g[4]),.k(h[
4]));

XNOR1
ans_bit5_unit(.j0(f[5]),.j1(g[5]),..k(h[
5]));

Endmodule

```

```

//module XNOR6 will find A XNOR B for
//every digit using module XNOR1.

```

```

//using XNOR1 module to get  $\sim(A \wedge B)$  for
//each digit.

```

```

module
full_Adder(a,b,cin,s,cout);

    input wire a, b, cin;

    output wire s, cout;


    assign s = cin ^ a ^ b;

    assign cout = (b & cin) | (a
& cin) | (a & b);
endmodule

```

//full adder adds a single bit digit and
//stores the sum in 's' and the carry digit
//in cout.

//cin is the initial carry which is set to 0.

//assigning 's' as : cin XOR a XOR b

//assigning 'cout'

```

module six_bit_adder(x,y,z);

```

// module 'six_bit_adder' adds up the six
//bit inputs and store the result in z.

```

    input wire[5:0] x,y;

```

//as the numbers are in 2's complement
//form we can set the result bit size to 6.

```

    output wire[5:0] z;

```

```

    wire[5:0] cinr;

```

//using full_adder module to get the sum
//and carry for each digit.

```

full_adder add_bit0(.a(x[0]),
.b(y[0]), .cin(1'd0), .s(z[0]),
.cout(cinr[0]));

```

//the carry for LSB is set to 0.

```

full_adder add_bit1(.a(x[1]),
.b(y[1]), .cin(cinr[0]), .s(z[1]),
.cout(cinr[1]));

```

//for further digits the 'cout' of the
//previous digit become the 'cin' for the
//following digit.

```

full_adder add_bit2(.a(x[2]),
.b(y[2]), .cin(cinr[1]), .s(z[2]),
.cout(cinr[2]));

```


```
full_adder add_bit3(.a(x[3]),  
.b(y[3]), .cin(cinr[2]), .s(z[3]),  
.cout(cinr[3]));
```

```
full_adder add_bit4(.a(x[4]),  
.b(y[4]), .cin(cinr[3]), .s(z[4]),  
.cout(cinr[4]));
```

```
full_adder add_bit5(.a(x[5]),  
.b(y[5]), .cin(cinr[4]), .s(z[5]),  
.cout(cinr[5]));
```


```
endmodule
```

CODE COMPILED SUCCESSFULLY:

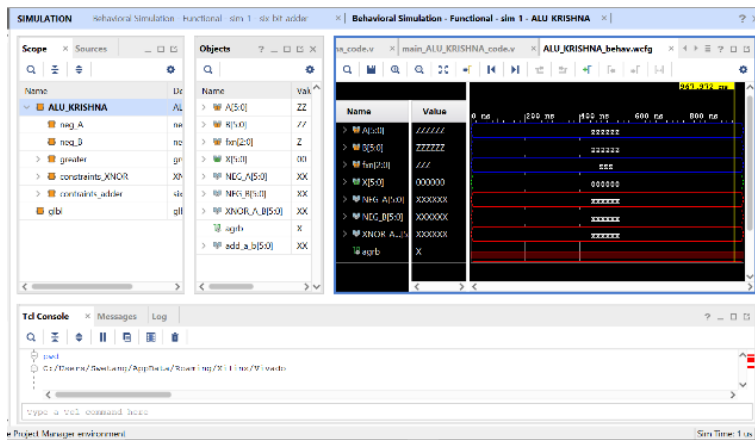


All module


Fxn = 000->

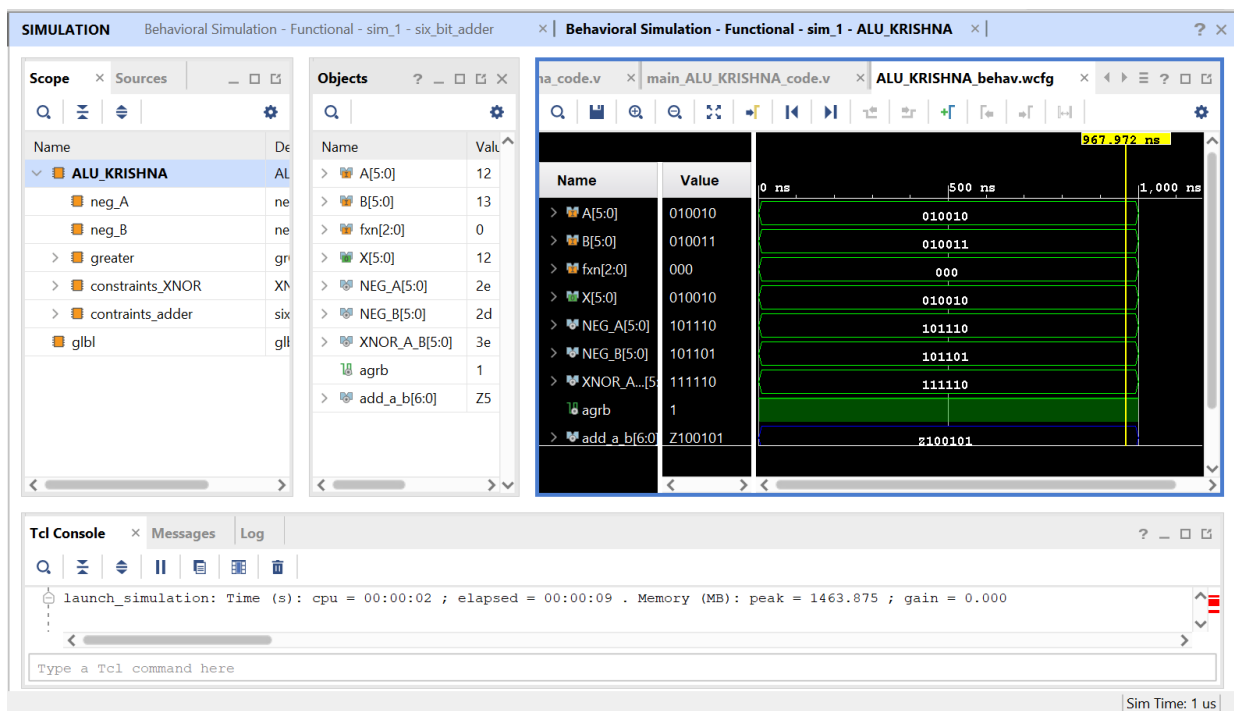


Fxn = 001->

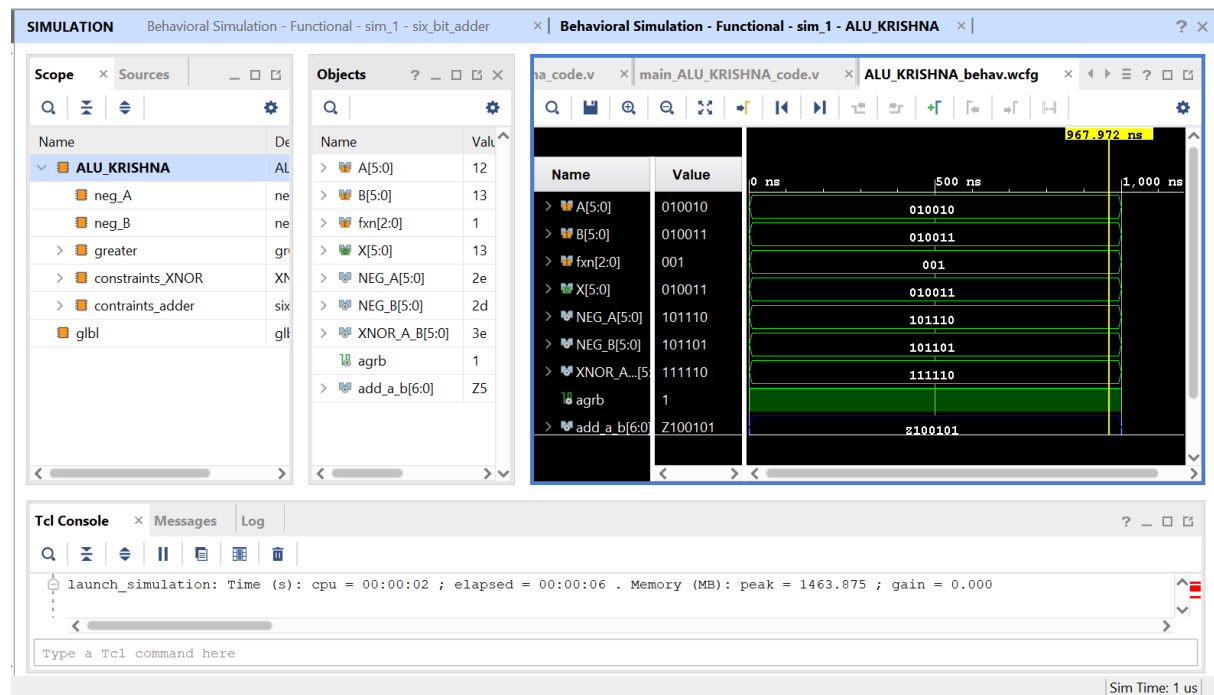


Fxn = 010->

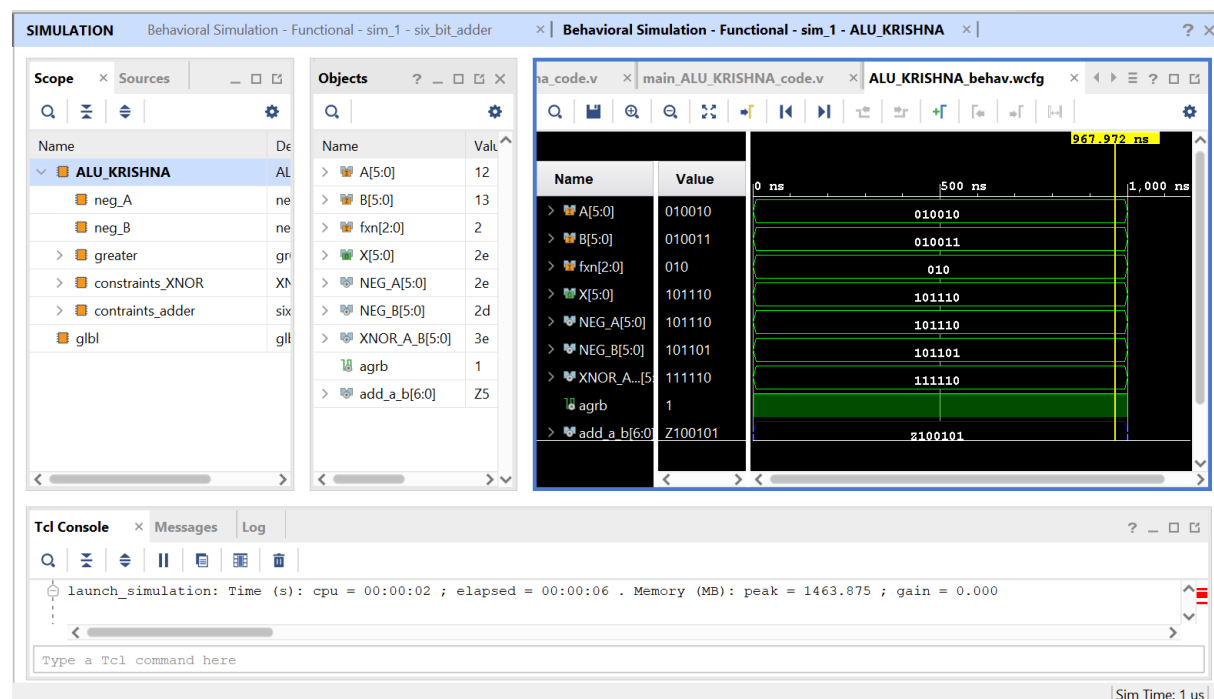


Fxn = 011->

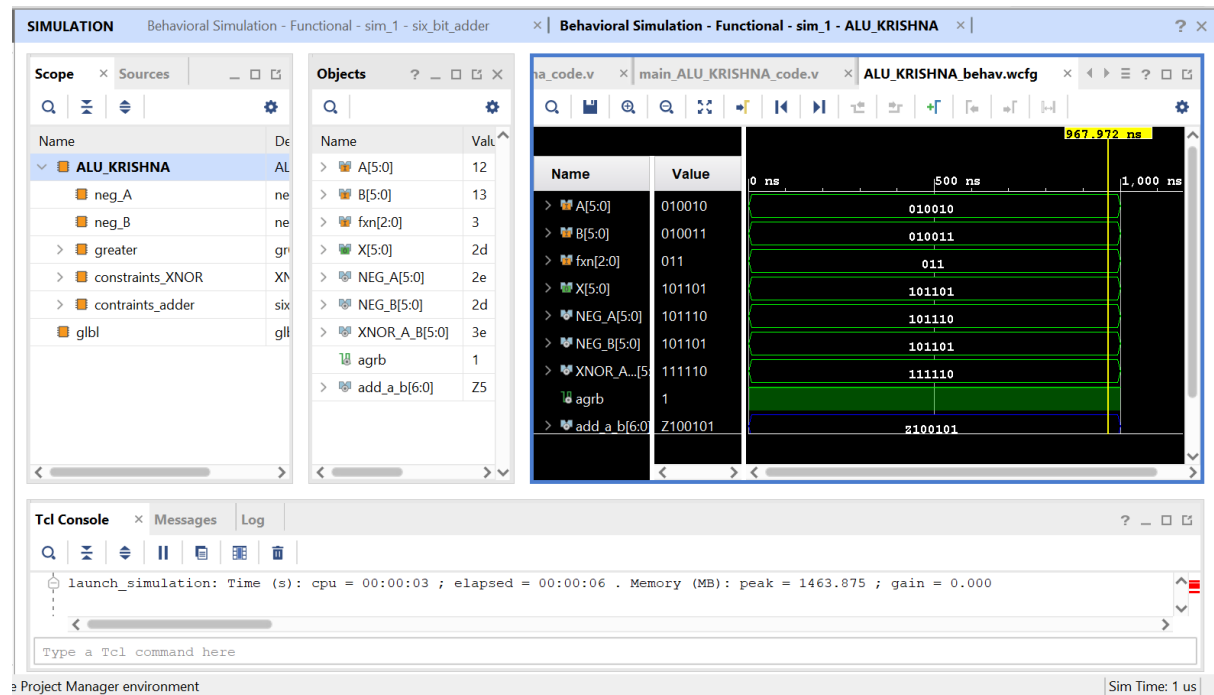


Fxn = 100->

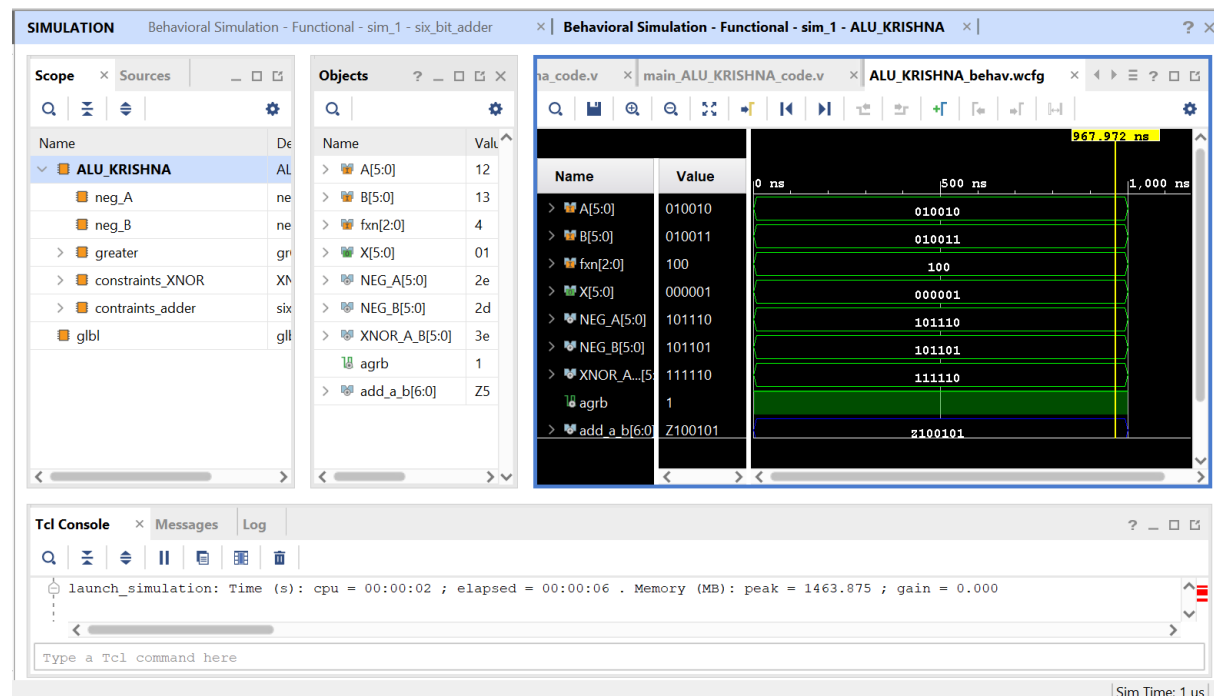

Fxn = 101->

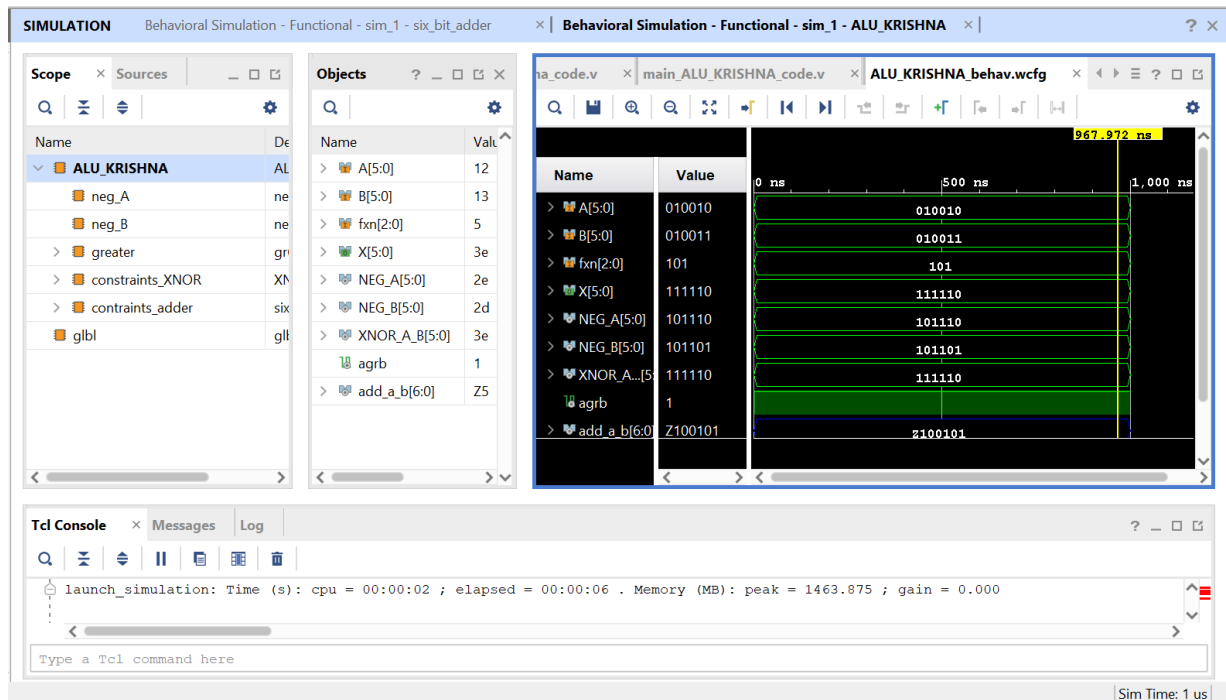

Fxn = 110->

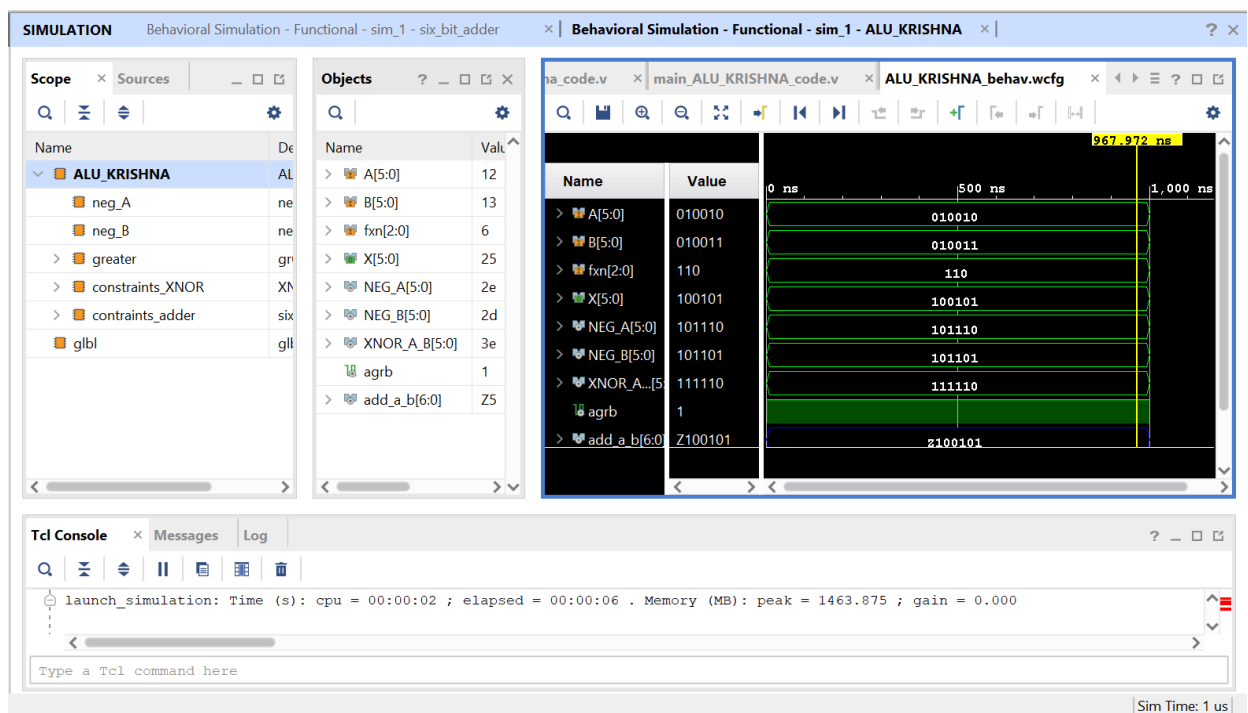

Fxn = 111->

SIMULATION Behavioral Simulation - Functional - sim_1 - six_bit_adder | Behavioral Simulation - Functional - sim_1 - ALU_KRISHNA

Scope Sources

Name | De

- ALU_KRISHNA
- neg_A
- neg_B
- greater
- constraints_XNOR
- constraints_adder
- glbl

Objects

Name | Value

- A[5:0] | 12
- B[5:0] | 13
- fxn[2:0] | 7
- X[5:0] | 3f
- NEG_A[5:0] | 2e
- NEG_B[5:0] | 2d
- XNOR_A_B[5:0] | 3e
- agrb | 1
- add_a_b[6:0] | Z5

ALU_KRISHNA_behav.wcfg

Name | Value

- A[5:0] | 010010
- B[5:0] | 010011
- fxn[2:0] | 111
- X[5:0] | 111111
- NEG_A[5:0] | 101110
- NEG_B[5:0] | 101101
- XNOR_A_B[5:0] | 111110
- agrb | 1
- add_a_b[6:0] | Z100101

0 ns | 500 ns | 1,000 ns

967.972 ns

Tcl Console Messages Log

launch_simulation: Time (s): cpu = 00:00:02 ; elapsed = 00:00:09 . Memory (MB): peak = 1463.875 ; gain = 0.000

Type a Tcl command here

Sim Time: 1 us

Testbench code:

```
module tb_Assign_Krishna();  
    reg[5:0] A,B;  
    reg[2:0] fxn;  
    wire[5:0] X;  
  
    ALU_KRISHNA A1(A,B,fxn,X);  
  
    initial  
    begin  
        A=6'b000001; B=6'b111111;  
        fxn= 3'b000;  
        #100;  
        A=6'b000001; B=6'b111111;  
        fxn= 3'b001;  
        #100;  
        A=6'b000001; B=6'b111111;  
        fxn= 3'b010;  
        #100;  
        A=6'b000001; B=6'b111111;  
        fxn= 3'b011;  
        #100;  
        A=6'b000001; B=6'b111111;  
        fxn= 3'b100;  
        #100;  
        A=6'b000001; B=6'b111111;  
        fxn= 3'b101;  
        #100;  
    end  
endmodule
```

//testbench module

//all the inputs will be taken as registers
//and the outputs as wire.

//using the main ALU module to test our
// design.

//using 6'bit binary input for testing //the
code.

//setting value of A as 1 and B as -1.
//following the tests for each 'fxn'.

```

        A=6'b000001; B=6'b111111;
fxn= 3'b110;

        #100;


        A=6'b000001; B=6'b111111;
fxn= 3'b111;

        #100;


end
endmodule

```

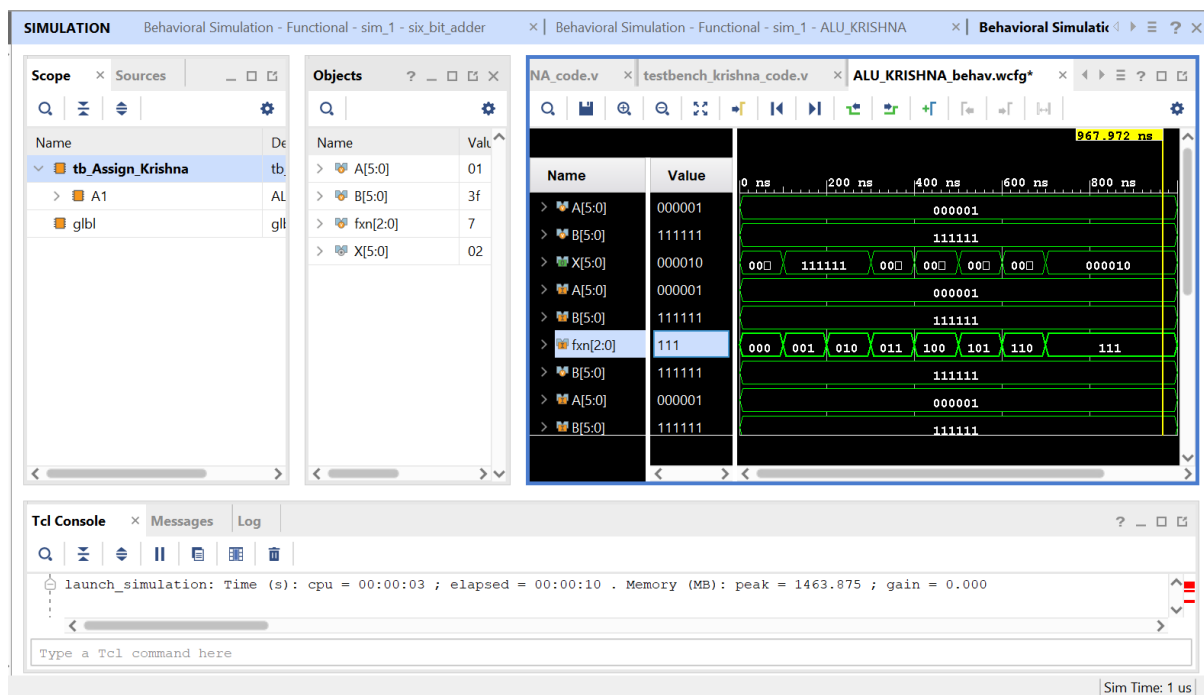
TESTBENCH RUNS SUCCESSFULLY
WITH ALL THE CORRECT OUTPUTS->




Testbench results:

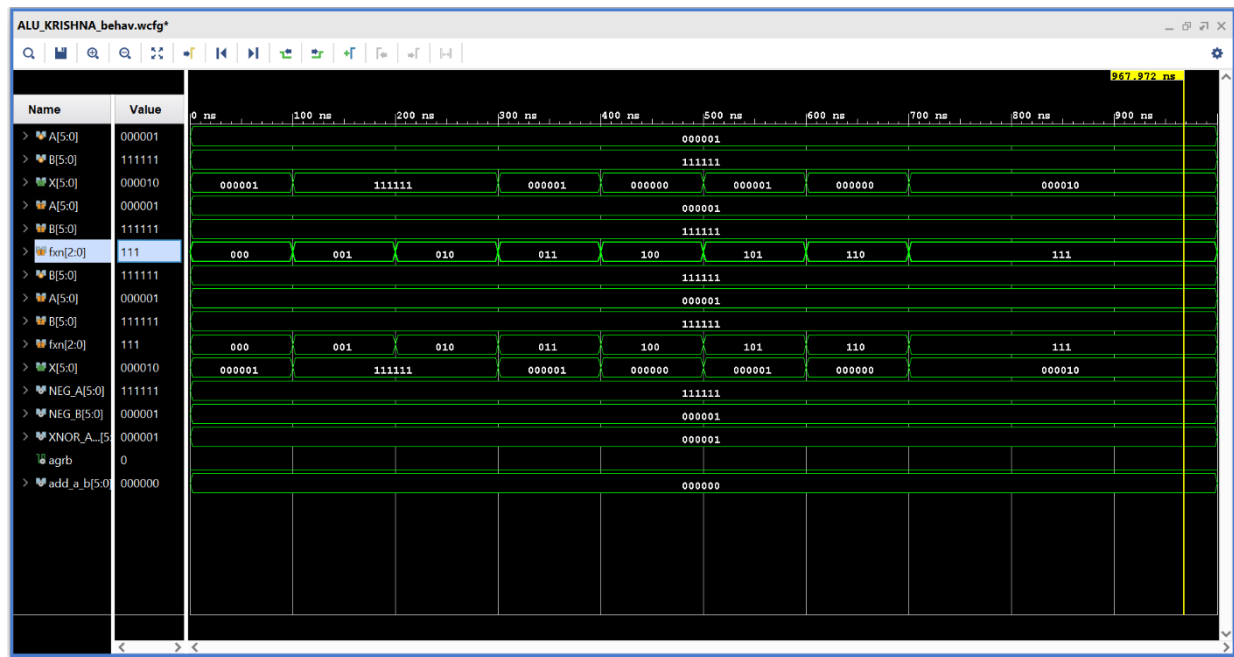

Screenshot (file directory structure):

 

DEMO:

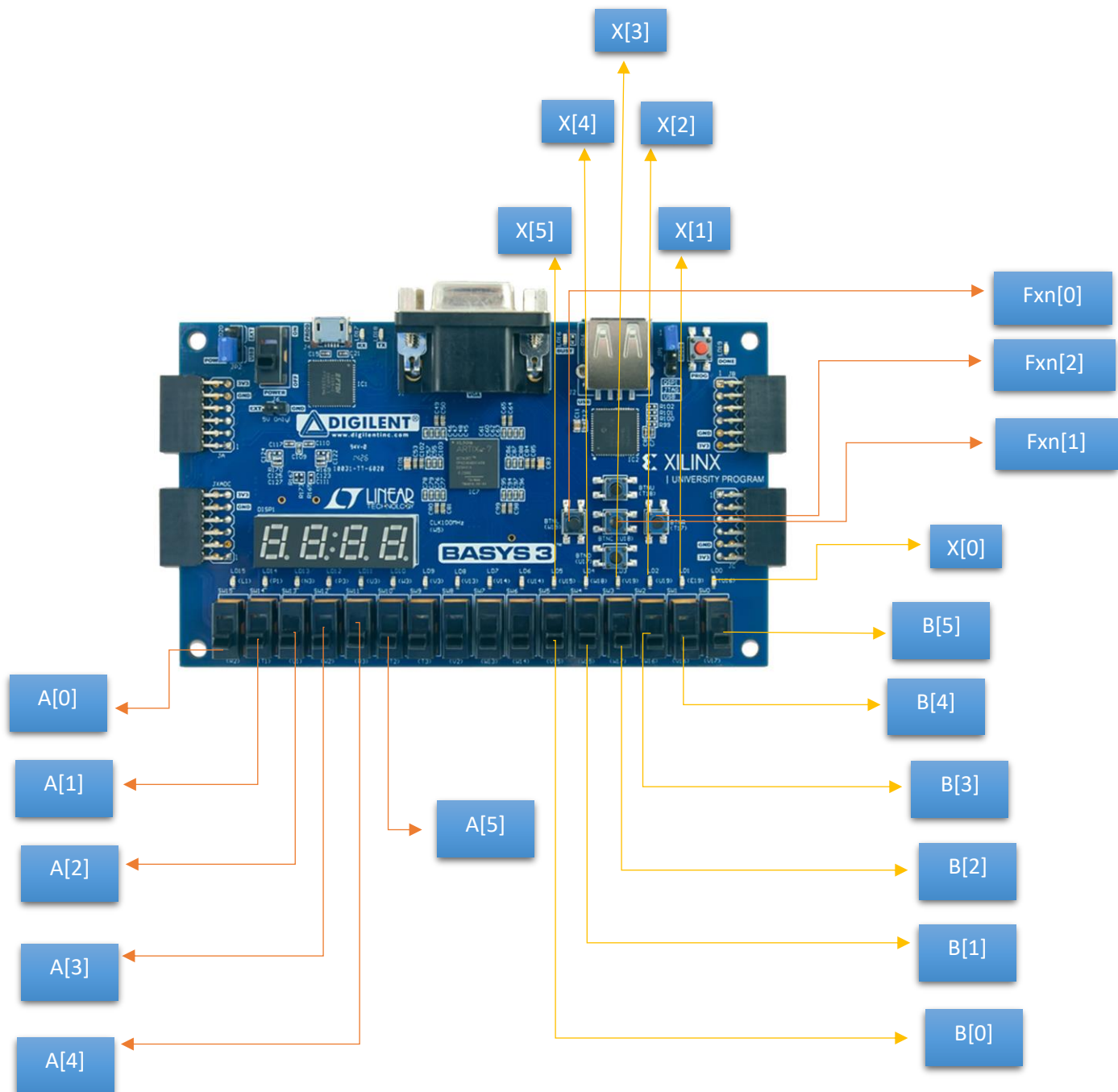

DEMO:

INPUT PINS:

##for inputs using the switches

##SWITCHES FOR A:

##A[0] = R2

##A[1] = T1

##A[2] = U1

##A[3] = W2

##A[4] = R3

##A[5] = T2

##SWITCHES FOR B:

##B[0] = V15

##B[1] = W15

##B[2] = W17

##B[3] = W16

##B[4] = V16

##B[5] = V17

##FOR fxn using buttons

BTNL for fxn[0] (pin - T17)

BTNC for fxn[1] (pin - V18)

BTNR for fxn[2] (pin - W19)

##LEDs for OUTPUT:

##X[0] =U16

##X[1] =E19

##X[2] =U19

##X[3] =V19

##X[4] =W18

##X[5] =U15

TO TEST THE PROGRAM ON BOARD, FOLLW THE STEPS:

The inputs A and B are assigned to switches so switch on sw5, sw4, sw3, sw2, sw1 and sw15 to give inputs 1 and -1 to A and B respectively.

The input fxn is assigned to buttons, press the button BTNR to give input value of 001 to fxn.

Now the expected output which must be shown in LEDs is 000001.

Similarly we can test it for the rest of the cases.

XDC FILE CODE:

```
#set_property PACKAGE_PIN W5 [get_ports CCLK]
#set_property IOSTANDARD LVCMOS33 [get_ports CCLK]
```

##using the LEDs to get the output stored in X.

##from LSB(X[0]) to MSB(X[5]) using LEDs 0-5.

```
set_property PACKAGE_PIN U16 [get_ports {X[0]}]
set_property IOSTANDARD LVCMOS33 [get_ports {X[0]}]
```

```
set_property PACKAGE_PIN E19 [get_ports {X[1]}]
set_property IOSTANDARD LVCMOS33 [get_ports {X[1]}]
```

```
set_property PACKAGE_PIN U19 [get_ports {X[2]}]
set_property IOSTANDARD LVCMOS33 [get_ports {X[2]}]
```

```
set_property PACKAGE_PIN V19 [get_ports {X[3]}]
set_property IOSTANDARD LVCMOS33 [get_ports {X[3]}]
```

```
set_property PACKAGE_PIN W18 [get_ports {X[4]}]
set_property IOSTANDARD LVCMOS33 [get_ports {X[4]}]
```

```
set_property PACKAGE_PIN U15 [get_ports X[5]]
set_property IOSTANDARD LVCMOS33 [get_ports X[5]]
```

##for inputs using the switches

##SWITCHES FOR:

##A[0] = R2

##A[1] = T1

##A[2] = U1

##A[3] = W2

##A[4] = R3

##A[5] = T2

set_property PACKAGE_PIN R2 [get_ports {A[0]}]

set_property IOSTANDARD LVCMOS33 [get_ports {A[0]}]

set_property PACKAGE_PIN T1 [get_ports {A[1]}]

set_property IOSTANDARD LVCMOS33 [get_ports {A[1]}]

set_property PACKAGE_PIN U1 [get_ports {A[2]}]

set_property IOSTANDARD LVCMOS33 [get_ports {A[2]}]

set_property PACKAGE_PIN W2 [get_ports {A[3]}]

set_property IOSTANDARD LVCMOS33 [get_ports {A[3]}]

set_property PACKAGE_PIN R3 [get_ports {A[4]}]

set_property IOSTANDARD LVCMOS33 [get_ports {A[4]}]

```
set_property PACKAGE_PIN T2 [get_ports {A[5]}]
set_property IOSTANDARD LVCMOS33 [get_ports {A[5]}]
```

##SWITCHES FOR:

```
##B[0] = V15
##B[1] = W15
##B[2] = W17
##B[3] = W16
##B[4] = V16
##B[5] = V17
```

```
set_property PACKAGE_PIN V15 [get_ports {B[0]}]
set_property IOSTANDARD LVCMOS33 [get_ports {B[0]}]
```

```
set_property PACKAGE_PIN W15 [get_ports {B[1]}]
set_property IOSTANDARD LVCMOS33 [get_ports {B[1]}]
```

```
set_property PACKAGE_PIN W17 [get_ports {B[2]}]
set_property IOSTANDARD LVCMOS33 [get_ports {B[2]}]
```

```
set_property PACKAGE_PIN W16 [get_ports {B[3]}]
set_property IOSTANDARD LVCMOS33 [get_ports {B[3]}]
```

```
set_property PACKAGE_PIN V16 [get_ports {B[4]}]
set_property IOSTANDARD LVCMOS33 [get_ports {B[4]}]
```

```
set_property PACKAGE_PIN V17 [get_ports {B[5]}]
set_property IOSTANDARD LVCMOS33 [get_ports {B[5]}]
```

##FOR fxn using buttons


```
## BTNL for fxn[0] (pin - T17)
## BTNC for fxn[1] (pin - V18)
## BTNR for fxn[2] (pin - W19)
```

```
set_property PACKAGE_PIN T17 [get_ports fxn[0]]
set_property IOSTANDARD LVCMOS33 [get_ports fxn[0]]
```


```
set_property PACKAGE_PIN V18 [get_ports fxn[1]]
set_property IOSTANDARD LVCMOS33 [get_ports fxn[1]]
```

```
set_property PACKAGE_PIN W19 [get_ports fxn[2]]
set_property IOSTANDARD LVCMOS33 [get_ports fxn[2]]
```


Outputs shown on board:

 

 
- inputs: OUTPUT:
- $A = 2$;
- $fxn = 110$; $X = 000011 = 3$;
- $B = 1$;



 
- inputs: OUTPUT:
- $A = 2$;
- $fxn = 110$; $X = 000011 = 3$;
- $B = 1$;



 - inputs: OUTPUT:
- A = 2;
- f_{xn} = 000; X = 000010 = 2;
- B = 1;



 - inputs: OUTPUT:
- A = 2;
- F_{xn} = 111; X = 000001 = 1;
- B = 1;



- inputs: OUTPUT:
- $A = 2;$
- $fxn = 010;$ $X = -2;$
- $B = 1;$

The design that I have created is using Multiplexer so if it gets any other unexpected input it would a default value output as 0.